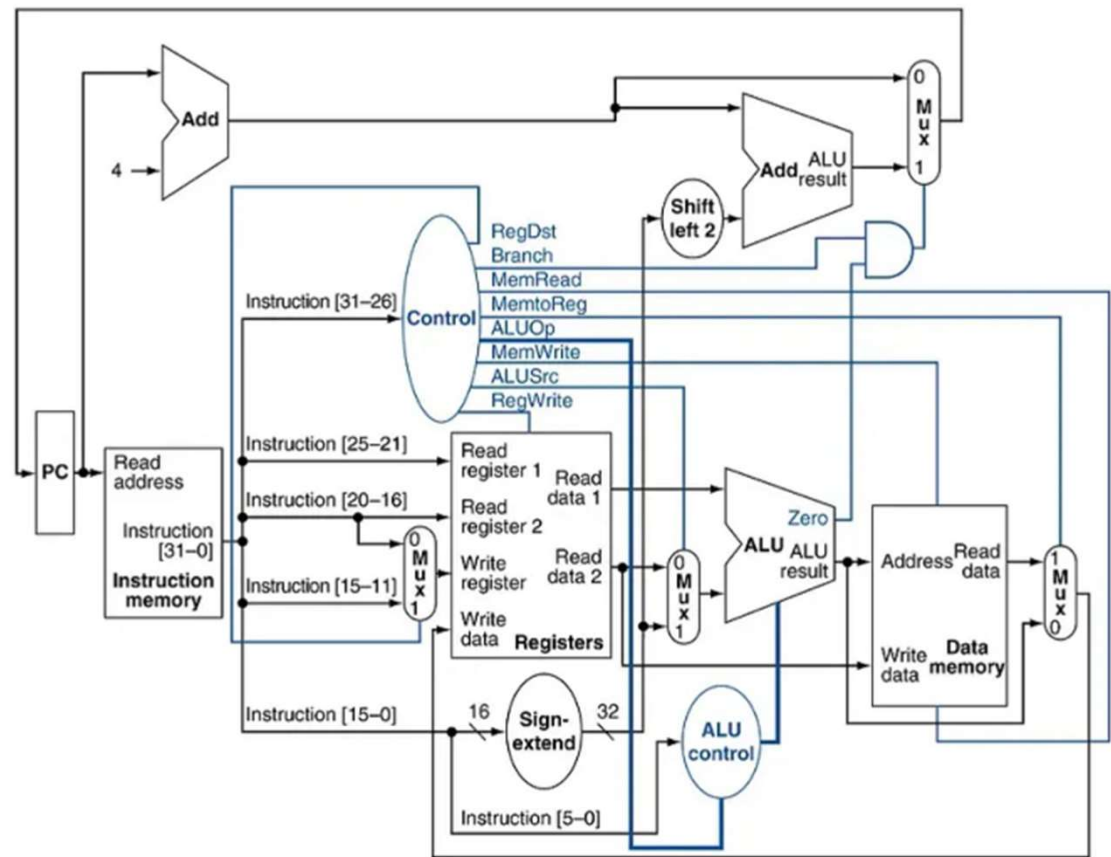


RISC-V Micro Processor

Block Diagram




Implemented instructions

	R Type	I Type	S Type
Use:	Register to Register	Immediate and loading ops	Storing operations
	Anything I can do in an ALU		
Code (ASM)	add x3, x1, x2	addi x5, x1, 10	sw x2, 4(x1)

Coming soon

B Type	U Type	J Type	M Extension
Conditional branching	Build large constants	Function calls / jumps	Hardware, multiply, divide, etc.
Uses two registers and an <i>immediate offset</i> to decide if the PC jumps	Loads a 20-bit immediate into upper bits of a register	Adds an immediate offset to PC and stores return address	Mostly can be done through the ALU
		Next to be implemented	

 

ALU

- It's a little absurd, the RTL

```

1 module Arithmetic_Unit (
2     input [31:0] A,
3     input [31:0] B,
4     input [3:0] ALU_Control,
5     output reg [31:0] ALU_Result,
6     output Zero
7 );
8     localparam ADD = 4'b0000;
9     localparam SUB = 4'b0001;
10    localparam AND = 4'b0010;
11    localparam OR = 4'b0011;
12    localparam XOR = 4'b0100;
13    localparam SLT = 4'b0101; // Set less than
14    localparam SLL = 4'b0110; // Shift left logical
15    localparam SRL = 4'b0111; // Shift right logical
16    localparam SRA = 4'b1000; // Shift right arithmetic
17    localparam STLU = 4'b1001; // Set Less Than Unsigned
18    always @(*) begin
19        case(ALU_Control)
20            ADD: ALU_Result = A + B;
21            SUB: ALU_Result = A - B;
22            AND: ALU_Result = A & B;
23            OR: ALU_Result = A | B;
24            XOR: ALU_Result = A ^ B;
25            SLT: ALU_Result = ($signed(A) < $signed(B)) ? 32'd1 : 32'd0;
26            SLL: ALU_Result = A << B[4:0];
27            SRL: ALU_Result = A >> B[4:0];
28            SRA: ALU_Result = $signed(A) >>> B[4:0];
29            STLU: ALU_Result = (A < B) ? 1 : 0;
30            default: ALU_Result = 32'd0;
31        endcase
32    end
33
34    assign Zero = (ALU_Result == 32'd0);
35 endmodule

```

Code

- The ALU code seems to me to be easier to understand than the full RTL Viewer
- This is where all R type instructions are done.
- A few I type instructions like ADDI,
- Most of the M extensions need to be added in



Registers


- All RegisterFile.v Does is create 32, 32 bit registers

RegisterFile.v

```

1 module RegisterFile (
2     input clk,
3     input reset,
4     input [4:0] rs1_addr,    // Read port 1 (5 bits = 32 regs)
5     input [4:0] rs2_addr,    // Read port 2
6     input [4:0] rd_addr,     // Write port
7     input [31:0] rd_data,    // Data to write
8     input reg_write,         // Write enable
9     output [31:0] rs1_data,  // Read data 1
10    output [31:0] rs2_data   // Read data 2
11 );
12
13 // Storage for 32 registers
14 reg [31:0] registers [0:31];
15
16 // Read ports: x0 always returns zero, others return stored value
17 assign rs1_data = (rs1_addr == 5'd0) ? 32'd0 : registers[rs1_addr];
18 assign rs2_data = (rs2_addr == 5'd0) ? 32'd0 : registers[rs2_addr];
19
20 // Write port: block writes to x0
21 always @(posedge clk) begin
22     if (reset) begin
23         integer i;
24         for (i = 0; i < 32; i = i + 1)
25             registers[i] <= 32'd0;
26     end
27     else if (reg_write && rd_addr != 5'd0)
28         registers[rd_addr] <= rd_data;
29 end
30 endmodule
31

```

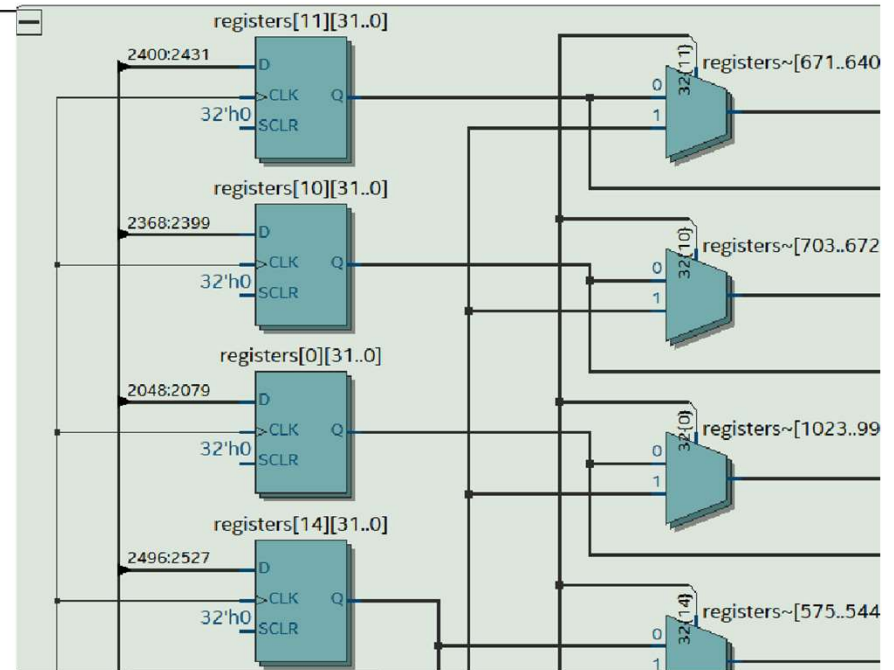

I and S types

- Primarily access the previously shown RegisterFile.v to read, write and perform quick actions

```

1  default_nettype none
2
3
4  module BranchUnit (
5      input [31:0] PC,           // Current program counter
6      input [31:0] rs1_data,     // Register rs1 value (for JALR)
7      input [31:0] immediate,   // Immediate value from instruction
8
9      output [31:0] branch_target, // Branch target: PC + imm
10     output [31:0] jump_target,   // JAL target: PC + imm
11     output [31:0] jalr_target,   // JALR target: (rs1 + imm) & ~1
12 );
13
14 // Branch and JAL: PC + immediate
15 // (Both use PC-relative addressing)
16 assign branch_target = PC + immediate;
17 assign jump_target = PC + immediate;
18
19 // JALR: (rs1 + immediate) with LSB cleared
20 // LSB must be cleared to ensure alignment
21 assign jalr_target = (rs1_data + immediate) & 32'hFFFFFFFE;
22
23 endmodule
24
25 `default_nettype wire

```

Program Counter and Branch Unit

- This is the frame work for the J commands and allow for the storing of

```

1  module ProgramCounter (
2      input MainClock,
3      input reset,           // Clear counter (renamed from ClearCounter)
4      input PCWrite,         // Enable PC update
5      input [1:0] PCSrc,     // Source select: 00=PC+4, 01=branch, 10=jump,
6      input [31:0] branch_target, // Branch target address
7      input [31:0] jump_target,   // Jump target address (JAL)
8      input [31:0] jalr_target,   // JALR target from ALU
9      output reg [31:0] PC       // Program Counter (32-bit for RISC-V)
10 );
11
12 // Internal signal for next PC value
13 reg [31:0] next_pc;
14
15 // Combinational logic for next PC calculation
16 always @(*) begin
17     case (PCSrc)
18         2'b00: next_pc = PC + 4;           // Normal: PC = PC + 4
19         2'b01: next_pc = branch_target;   // Branch taken
20         2'b10: next_pc = jump_target;     // JAL
21         2'b11: next_pc = jalr_target;     // JALR
22         default: next_pc = PC + 4;
23     endcase
24 end

```

Additional Notes

- The FSM design from lab 8 is being kept around. Same 4 phases of Fetch (stage 1), Decode (stage 2), Execute A (stage 3), Execute B (stage 4).
- I have a very poorly made main I didn't feel like showing.